

Minesweeper Project

Alexis Le Glaunec (afl5), Agha Sukerim (ads13), Liam Waite (lcw6)

1-paragraph:

Minesweeper is a chip implementation of the [Minesweeper game](#), in which the goal is to clear the board without detonating mines. Initially, 1-3 mines are placed using a pseudo-random algorithm in a 3x3 grid. Then, the user can input a position by choosing a number between 1 and 9 on a [keypad switch](#). The chip will respond with a color on a LED dot matrix screen encoding the following information: red if it hits a mine (and the game ends), green if there is no mine among the 3-8 neighbors of the position and yellow if there is at least one mine in the position neighbors. If the position is yellow, a digital screen displays how many mines are adjacent. The initially unlit dot matrix screen will record and color in each position that is visited. The player wins if it clears all cells but the ones with mines. The chip will have the ability to remember the score, support game over and restart the game.

Overview

In this project, we propose an implementation of the Minesweeper game, where a player tries to clear the 3x3 board without detonating mines. The user input `data_in` is a 4-bit signal to encode all of the board cells (ranging from 0 to 8 in a row-first arrangement).

Registers

Our design requires 3 internal registers: three 4-bit registers of `mines` to store the mines' positions, with it being 0000 if a mine is not used. A 9-bit register called `cleared` is used to store the cells that have been cleared by the user (where “1” at position k means cell k is `cleared`), and a 4-bit register `score` is used to store the current score (i.e. number of cells cleared in the game). A 32-bit register `total_score` is used to store the cumulative score throughout all of the games. In total, we would need $4 \times 3 + 9 + 4 + 32 = 57$ bits of memory and 6 registers.

Finite State Machine and ALU

At every step, the user inputs a 4-bit value and we compare it against the mine position by performing a bitwise-and operation (`data_in & mine` for all mines). If $(\text{data_in} \& \text{mine}) \neq 0$, then the game is over (as displayed on the screen) and the user can restart the game with a `rst` signal (in practice, a button). Otherwise, we record the cleared cell by updating the cleared register. Since `cleared` stores each position by bit while `data_in` stores the numbered position in binary, we will have to first convert `data_in` with a decoder (e.g. `data_in` = 0011 -> `data_inConverted` = 000000100). We can then record the cleared cell by updating the cleared register as follows: `cleared := cleared | data_in`. We also increment both the `score` and `total_score`. Then, the game goes on. If `cleared` is all-ones, the game is over, the user wins, and again the user can decide to start a new game using the reset button. Mine positions are automatically recorded in the `cleared` register for this to work. When the game is over, we reset all the registers except for `total_score`. In practice, implementing those operations requires the ALU to contain an increment unit, a 9-bit bitwise-AND, a 9-bit bitwise-OR, and a decoder.

I/O

The design would require 5 input pins for the 4-bit user input signal and the `restart` signal. The outputs include a 3x3 LED matrix and an I²C display. The LED matrix would only need 6 outputs and multiplexing to control each row and column in order to light specific LEDs. For the display that outputs the number of nearby mines, it would only require 2 pins. In total, we expect to use 12 I/O pins.


Scalability

The game is by nature scalable; we can increase the board size which will result in larger registers and larger user input word size to fully utilize the chip area. There will be different levels consisting of a varying number of mines at the start of the game.

Testing


We intend to test our design at each step with testbenches simulating games with a series of user actions. In addition, we will incorporate SVA to catch any inconsistencies. We will unit test separately the components of the ALU.

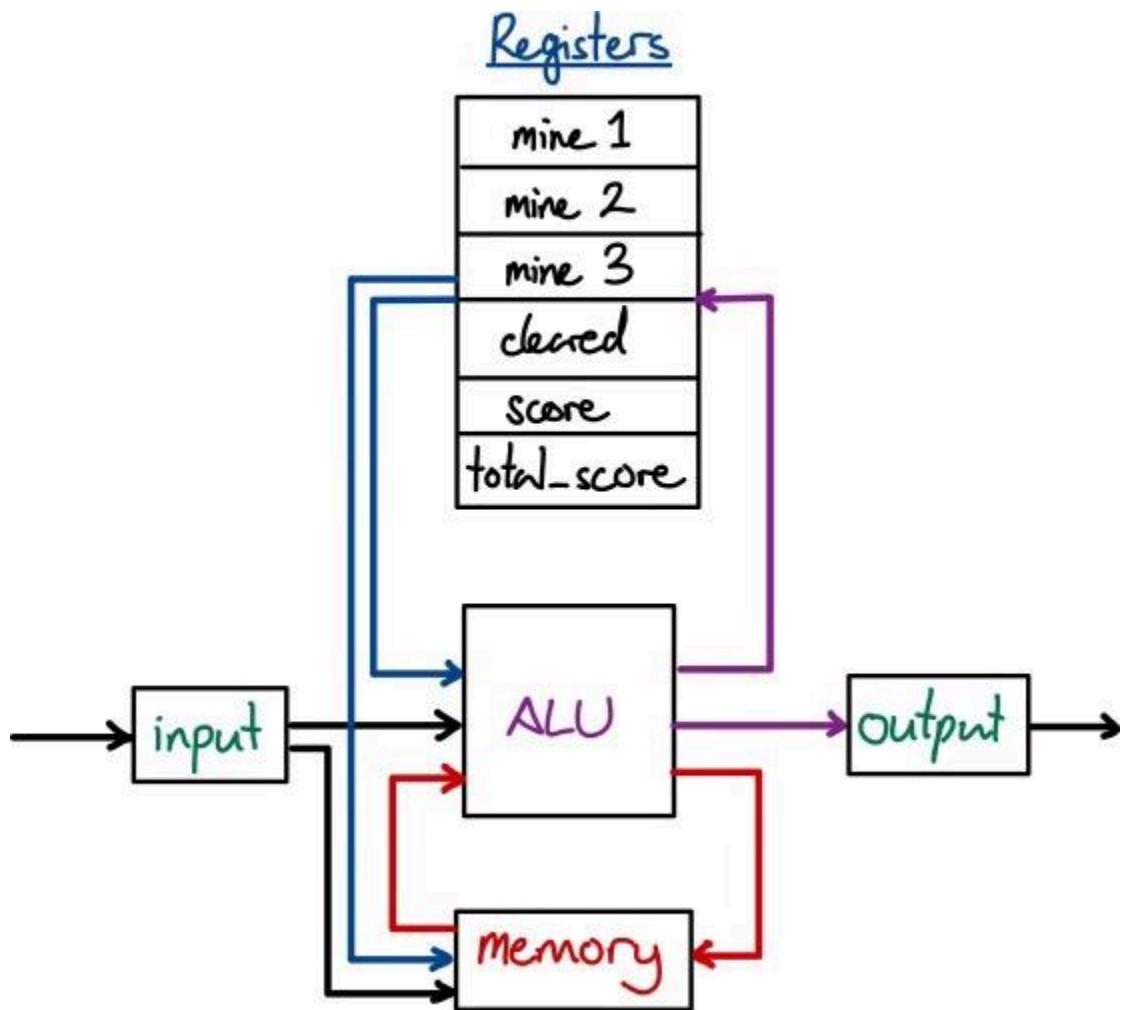Intermediary Block Diagram (see below for complete)




Schematics of the ALU

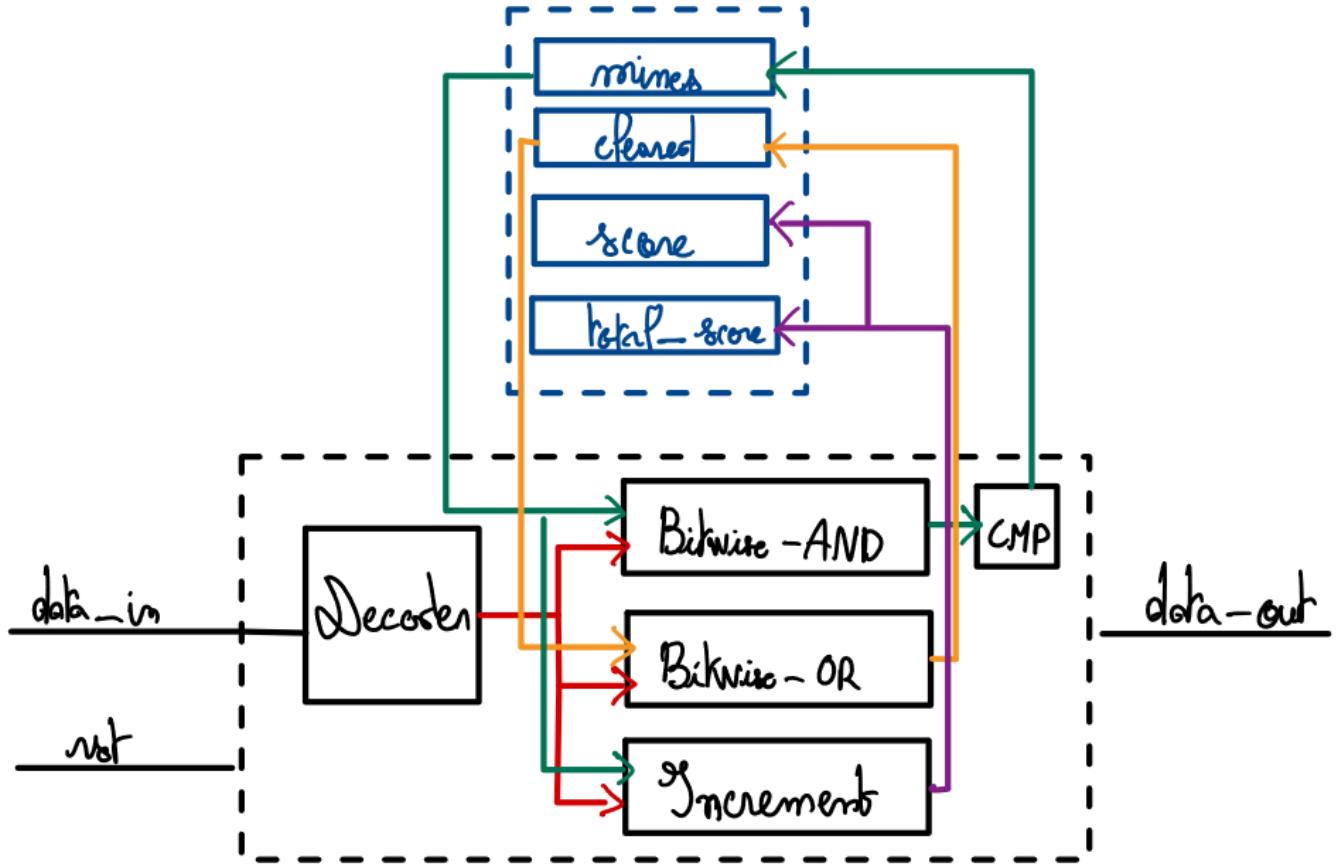This diagram shows more details about the inside of the ALU, and how it would interconnect with the registers.



Bubble Diagram

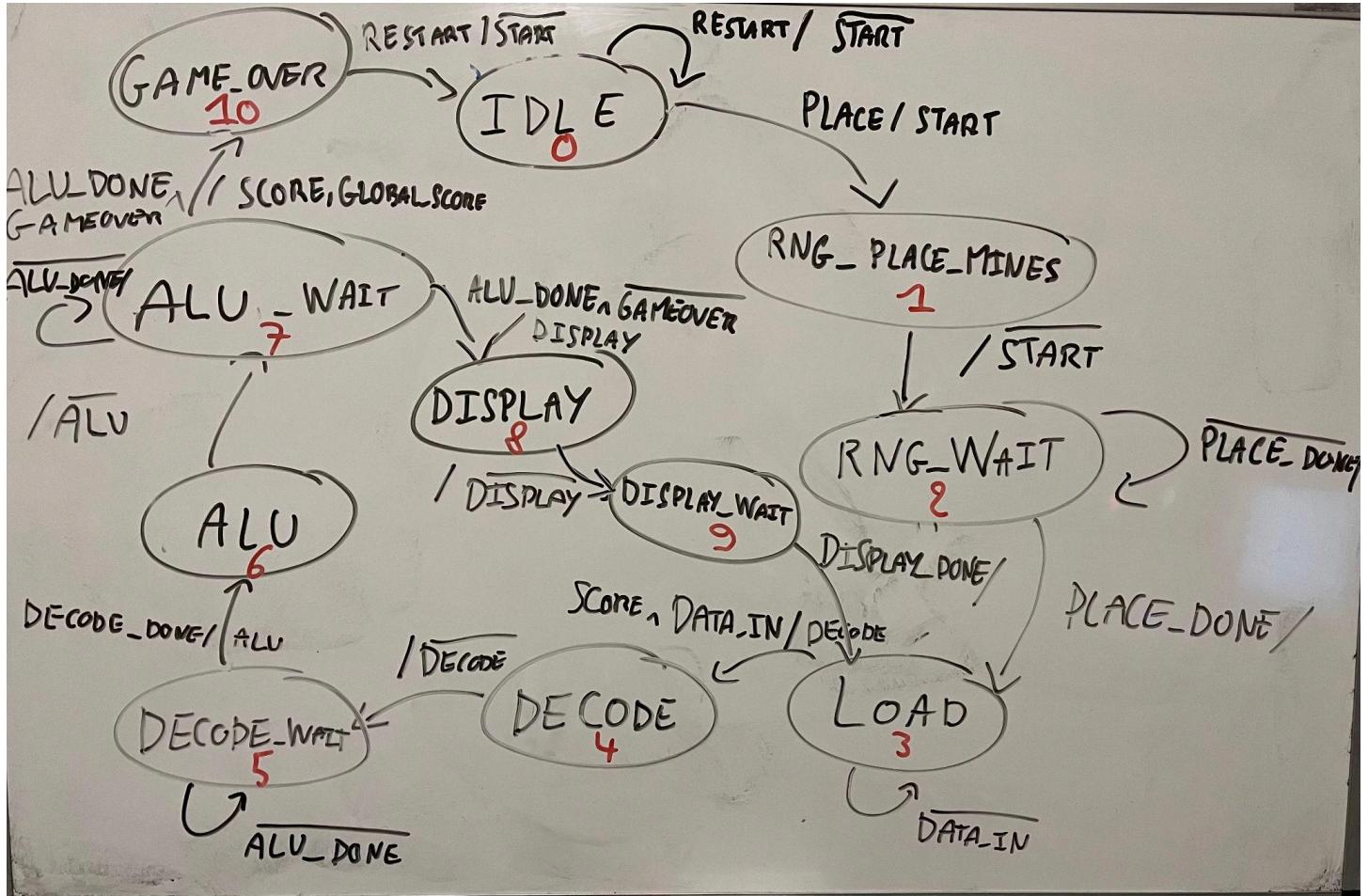

In this diagram, we call four distinct data paths:

1. RNG: random number generator to place the mines (number depending on the level chosen)
2. DECODE: decode the user input into a bitmask
3. ALU: perform the arithmetic operations (bitwise-and, bitwise-or, increment)
4. DISPLAY: display the cleared cells and indicate how many mines are nearby the last cleared position


For the ALU, we would use a second FSM consisting of 3 stages:


1. Bitwise-and to compute `data_in & mine` (to know if the user detonated a mine)
2. Bitwise-or to keep track of the cleared cells
3. Increment to increment the score (based on number of cleared cells)

Each step consists of 1 state. So, in total (main_FSM + ALU_FSM), we end up with 13 states.

Block Diagrams

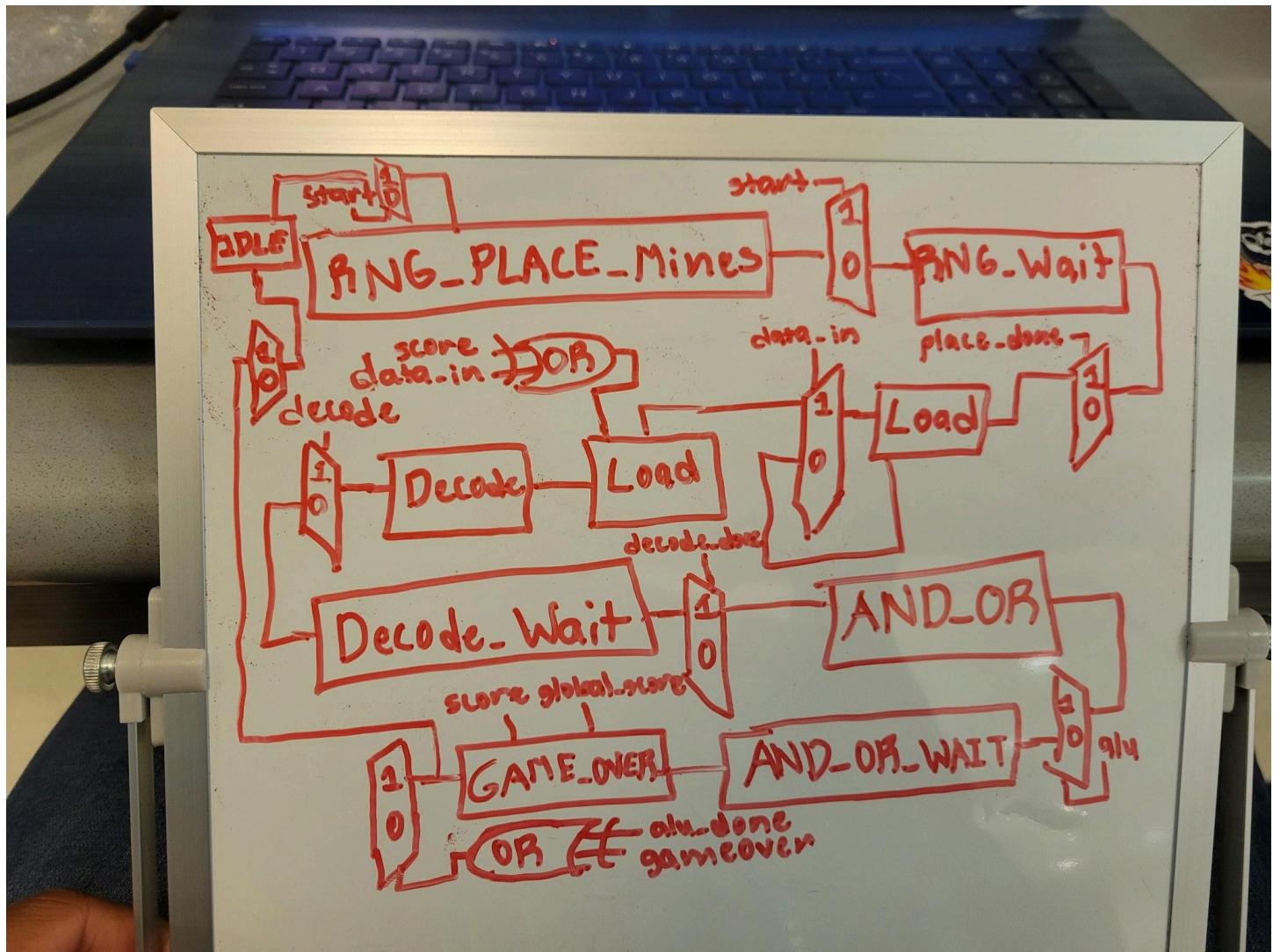We have designed the block diagrams for the ALU and the FSM:



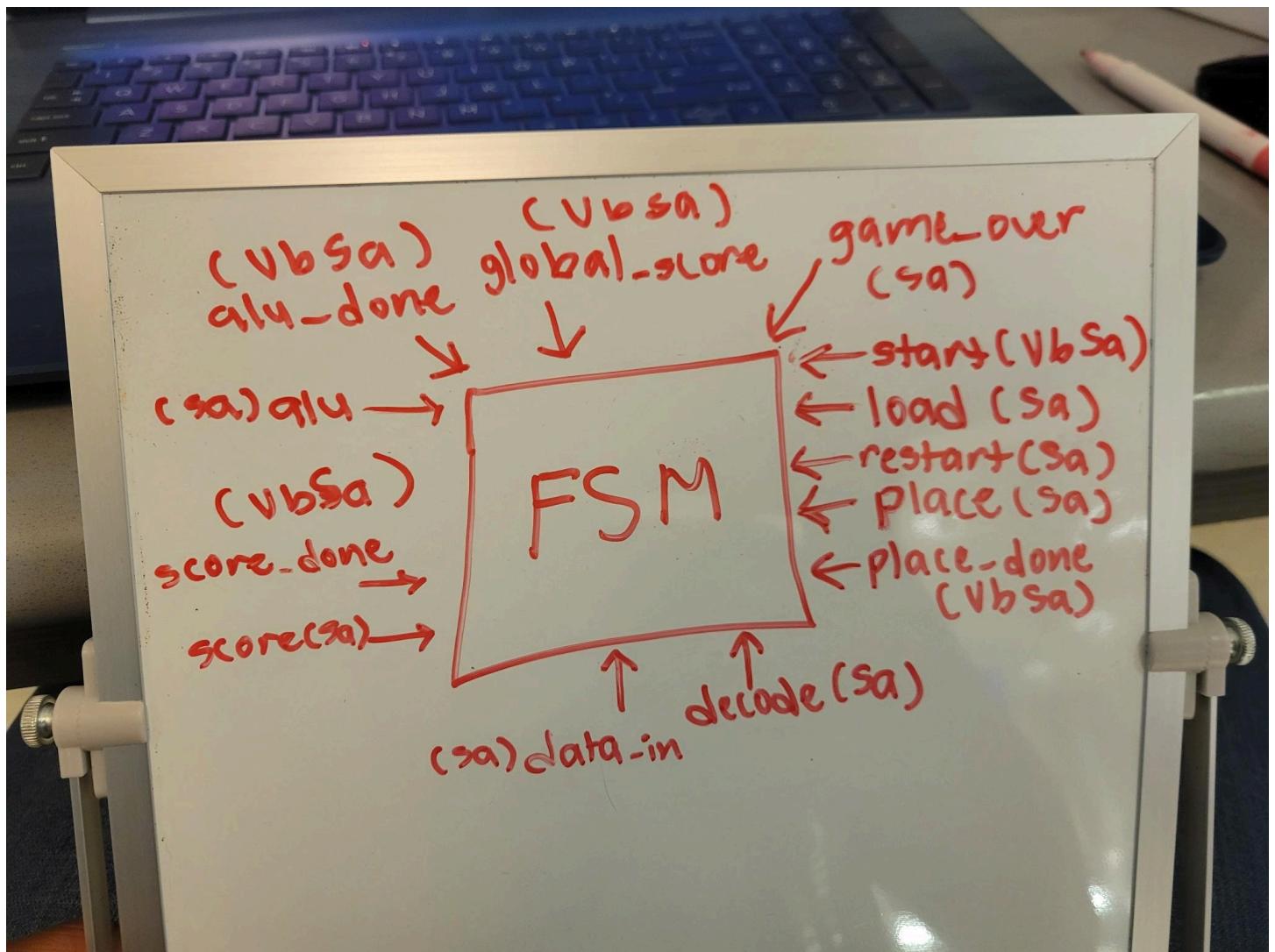

FSM Pseudo-Code

1. module Minesweeper(
 - 1.1. input wire [3:0] data_in, //4-bit input for user cell selection
 - 1.2. input wire [3:0] reset, // RESET signal
 - 1.3. output wire [5:0] led_matrix, // Output for 3x3 LED matrix
 - 1.4. output wire [1:0] nearby,
 - 1.5. output wire [4:0] score); // Output for I2C display
2. Internal Registers
 - 2.1. reg [3:0] mine1, mine2, mine3
 - 2.2. reg [8:0] cleared
 - 2.3. reg [3:0] score
 - 2.4. reg [31:0] total_score
3. Internal Constants
 - 3.1. parameter IDLE = 0
 - 3.2. parameter RNG_PLACE_MINES = 1
 - 3.3. parameter RNG_WAIT = 2

- 3.4. parameter LOAD = 3
 - 3.5. parameter DECODE = 4
 - 3.6. parameter DECODE_WAIT = 5
 - 3.7. parameter AND_OR = 6
 - 3.8. parameter AND_OR_WAIT = 7
 - 3.9. parameter GAME_OVER = 8
 - 3.10. parameter WIN = 9
4. Internal Variables
- 4.1. reg [2:0] state
 - 4.2. reg [2:0] next_state
5. Decoder
- 5.1. wire [8:0] data_inConverted
 - 5.2. Decoder4to9 decoder(data_in,data_inConverted)
6. ALU Operations
- 6.1. wire mine_detected //decides if game is over
 - 6.2. assign mine_detected = *compare data_in and all mine1, mine2, mine3, assigning HIGH if any AND is HIGH*
7. Random Mine Placement Generator
- 7.1. Simple algorithm to generate three 4-bit positions for mine1, mine2, mine3
 - 7.2. Check that mine1 != mine2 != mine3, or do again
 - 7.3. output place_done
8. FSM Logic
- 8.1. *High 'reset' input all return to IDLE*
 - 8.2. IDLE
 - 8.2.1. If (~reset): next_state = RNG_PLACE_MINES
 - 8.3. RNG_PLACE_MINES
 - 8.3.1. Start Random Mine Placement Generator
 - 8.3.2. next_state = RNG_WAIT
 - 8.4. RNG_WAIT
 - 8.4.1. If (~place_done): next_state = LOAD
 - 8.5. LOAD
 - 8.5.1. If (mine_detected): next_state = GAME_OVER
 - 8.5.2. If (~mine_detected): next_state = DECODE
 - 8.6. DECODE
 - 8.6.1. To decode data_in to data_inConverted
 - 8.6.2. If (~mine_detected): next_state = DECODE_WAIT
 - 8.7. DECODE_WAIT
 - 8.7.1. If data_inConverted is new, next_state = AND_OR
 - 8.8. AND_OR
 - 8.8.1. Update 'cleared' with 'data_inConverted' (cleared := cleared | data_in)
 - 8.8.2. If (cleared == 9b1), next_state = WIN
 - 8.8.3. If not, next_state = LOAD
 - 8.9. GAME_OVER

- 8.9.1. If (reset): next_state = IDLE
 8.10. WIN
 8.10.1. If (reset): next_state = IDLE
9. Decoder4to9
 9.1. Function/module to convert 4-bit data_in position to 9-bit position

```
// FSM Logic
always @(posedge rst or posedge data_in) begin
  if (rst) begin
    // Reset logic, except total_score
    state <= IDLE;
    cleared <= 0;
    score <= 0;
    // Mines should be randomly assigned in a practical implementation
  end else begin
    case(state)
      IDLE: next_state <= CHECK_MINE;
      CHECK_MINE: begin
        if (mine_detected) next_state <= GAME_OVER;
        else next_state <= UPDATE_SCORE;
      end
      UPDATE_SCORE: begin
        if (cleared == 9'b111111111) next_state <= WIN;
        else next_state <= IDLE;
      end
      GAME_OVER: begin
        // Reset all except total_score
        next_state <= IDLE;
      end
      WIN: begin
        // Increment total_score and reset for a new game
        total_score <= total_score + score;
        next_state <= IDLE;
      end
    endcase
  end
end

// Sequential Logic for state transition
always @(posedge clk) begin
  state <= next_state;
  case(state)
    CHECK_MINE: begin
      // Game over logic
    end
    UPDATE_SCORE: begin
      cleared <= cleared | data_inConverted;
    end
  endcase
end
```

```
score <= score + 1;
total_score <= total_score + 1;
end
GAME_OVER: begin
    // Game over logic
end
WIN: begin
    // Win logic
end
endcase
end


// Output Logic (simplified for pseudocode)
// Actual implementation would control the LED matrix and I2C display

endmodule

module Decoder4to9(input [3:0] in, output reg [8:0] out);
    always @ (in) begin
        out = 1 << in;
    end
endmodule
```

Controller FSM

Bubble diagram:

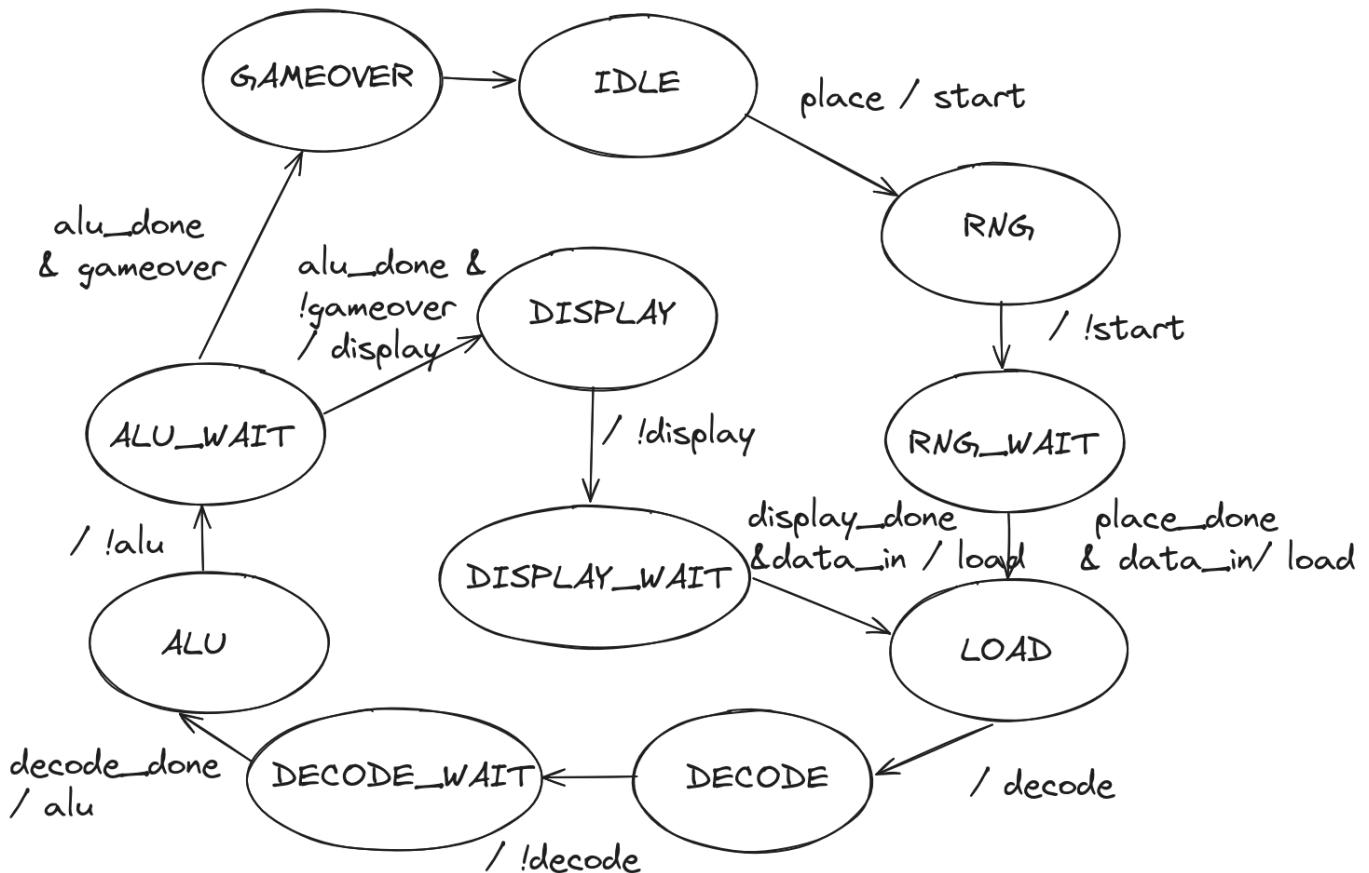

We have updated the Bubble diagram to better fit the use case for the Minesweeper game by adding signals that were missing in the previous iterations. We also took into account the remark about the levels, by increasing the grid to 5x5 (25 cells) to allow for more difficulty adding mines. Please note that in order to keep the bubble diagram readable, we do not represent self-loops. Those can be deduced to be the default edge taken if no other is available.

For the next milestone, we plan on simplifying the diagram by removing the unnecessary handshake for the decoding as it only takes 1 cycle. Furthermore, we have started implementing the logic for the data path and RNG, but it is not finished yet.

Verilog code is attached to this document.

Testbench:


Our testbench consists for now in two rounds of the minesweeper game:

1. At cycle 2, we restart the FSM
2. At cycles 3 and 4, we generate the mine using RNG (handshake with rng.v)
3. From cycle 5 to cycle 13, we run one iteration of the game, loading the user input (clearing cell 2) up to the display of the board. As there is no mine on cell 2, we continue the game


4. From cycle 14 to cycle 21, we run the second iteration of the game, loading the user input (clearing cell 5). As there is a mine on cell 5, we go to gameover state.

This testbench is a proof-of-concept for our design. We plan to extend the testbench to the scenario of winning, i.e. clearing all the mines to have more extensive testing.

Questa:

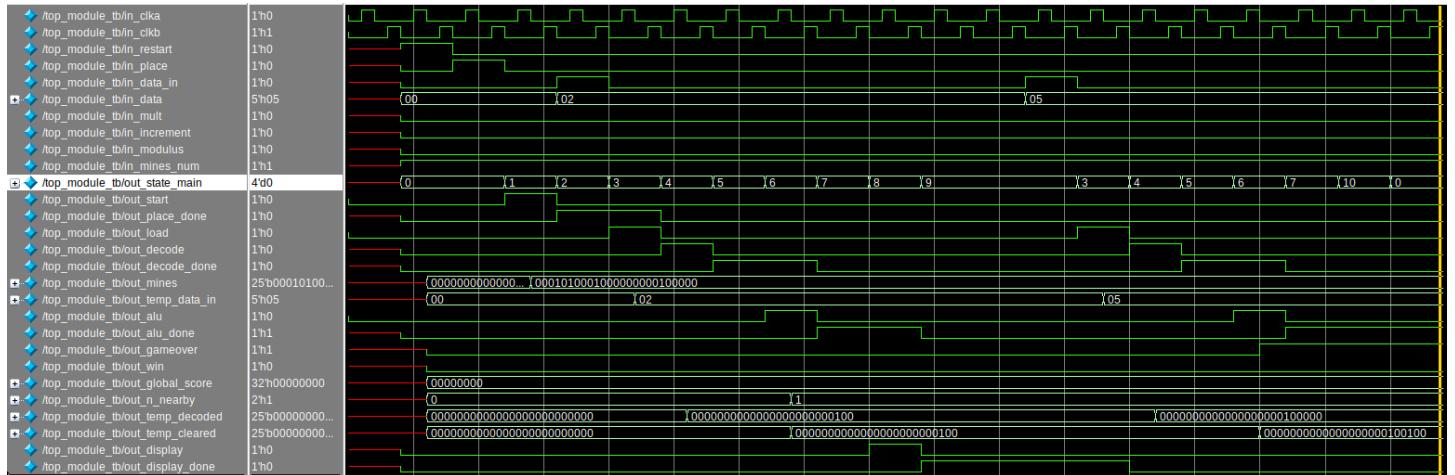

Questa post DC:

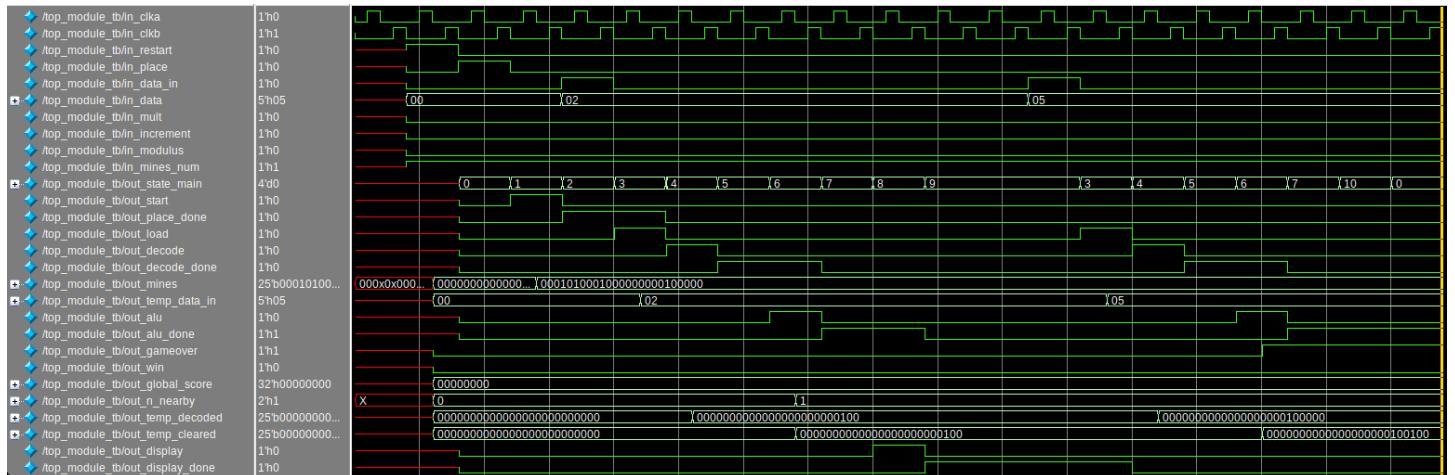

We observe no difference in the testbench behavior between before and after synthesis.